

Real-time digital simulation of analog audio effects

Brno University of Technology

28/10/2011

Outline

- Introduction and motivation
- Linearized audio effect modeling
- Analog phaser effect example
- Nonlinear audio effect modeling
- Guitar tube preamp
- Sound examples

Introduction and motivation (1)

- Electronic circuit simulators have been available since 1973 – SPICE (Simulation Program with Integrated Circuit Emphasis)
 - **Universal tool** for all kinds of electronic circuits
 - Nodal analysis of the **whole electronic circuit**
 - **Focus on simulation accuracy** (complex electronic device models)
 - Transient analysis (time-domain large-signal solution of nonlinear differential algebraic equations) – numerical algorithms
 - Solution can be used unstable with wrong simulation setup
 - Waveform input in the latest versions
 - **Not suitable for real-time processing of audio signals due to high computational complexity** especially on common personal computers

Introduction and motivation (2)

- Audio effects and amplifiers (guitar amplifiers)
 - Use **limited** library of electronic components
 - There is limited number of circuit topologies (especially for guitar amplifiers)
 - The circuit schematic can be splitted to several parts according to their function
 - Some parts can be omitted – e.g. power supply circuit
 - Some parts can be linearized – e.g. filters
 - Some parts can be simplified – e.g. oscillators
 - Work in audible region of frequencies (we don't care about high frequency signals)


Introduction and motivation (3)

- Algorithms for real-time simulation of analog audio effects
 - **The goal is to reduce computational complexity as much as possible while the auditory perception remains the same**
 - Can exploit properties from the previous slide
 - Simplified electronic component models (freq. region 20 Hz – 20 kHz)
 - Division into blocks and simplification of the circuit
 - Linear versus nonlinear blocks
 - Approximations
 - Masking effect
 - Math functions instead of circuits (summation)

Linearized models of analog effects


- Quite a lot of analog effects can be linearized
 - Passive electronic circuits
 - Circuits with operational amplifiers in certain range of output voltages (bellow power supply)
- Linearized models can be described by transfer function $H(s)$
- Discretization (e.g. bilinear transform)
- Implementation using digital linear filters

Example – Analog phaser effect

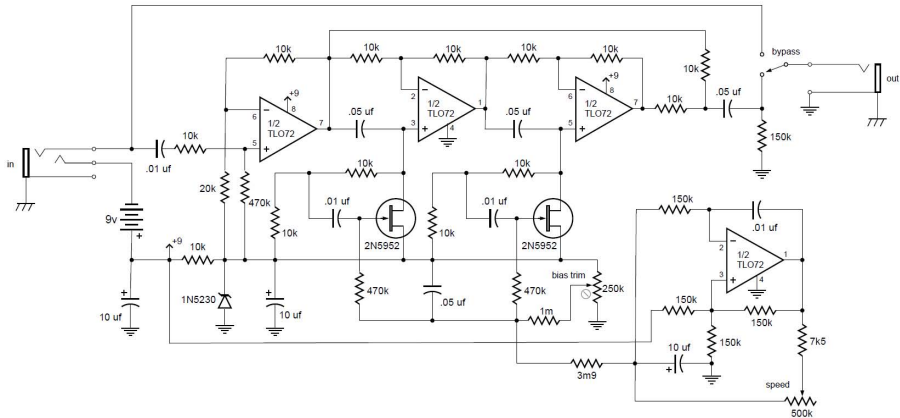


Analog phaser effect – Simulation


- Simulation using nodal analysis
 - cca 40 circuit nodes \rightarrow 40 circuit equations
 - nonlinear solver
 - at least one matrix inversion in each signal sample
 - high computational complexity
- Simulation optimized for real-time processing
 - division into smaller and more simple blocks that are solved individually
 - connection of the blocks with respect to mutual interaction – the input and output impedance have to be matched
 - each block must include output impedance from previous block and input impedance from following block

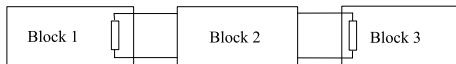


Analog phaser effect – the whole circuit

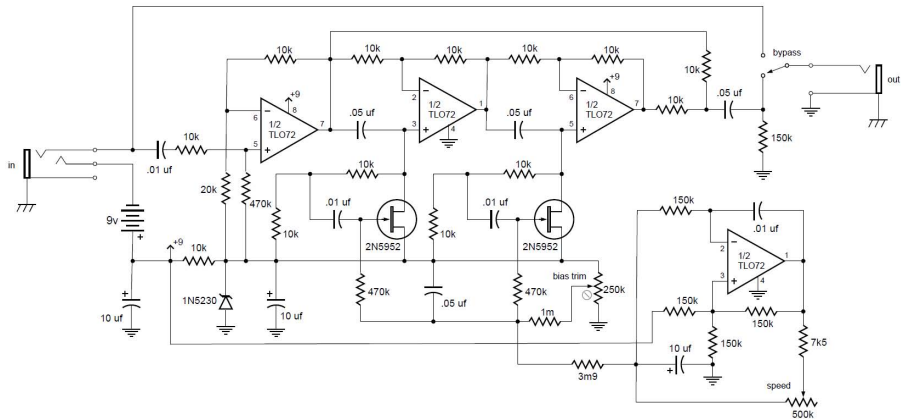

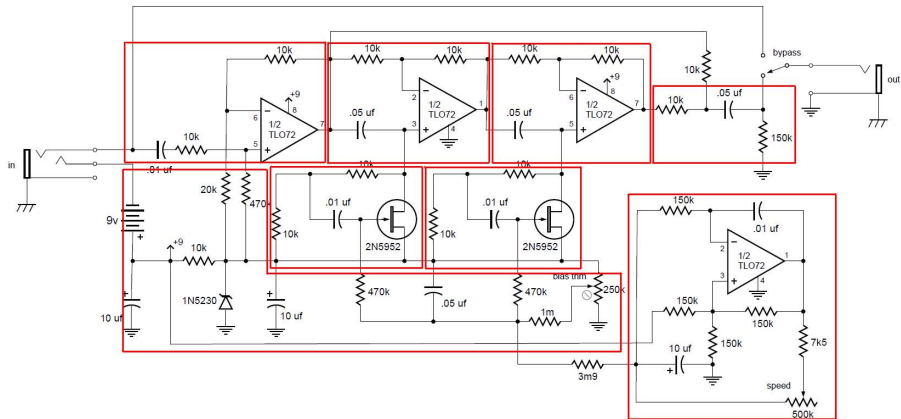Analog phaser effect – division into blocks




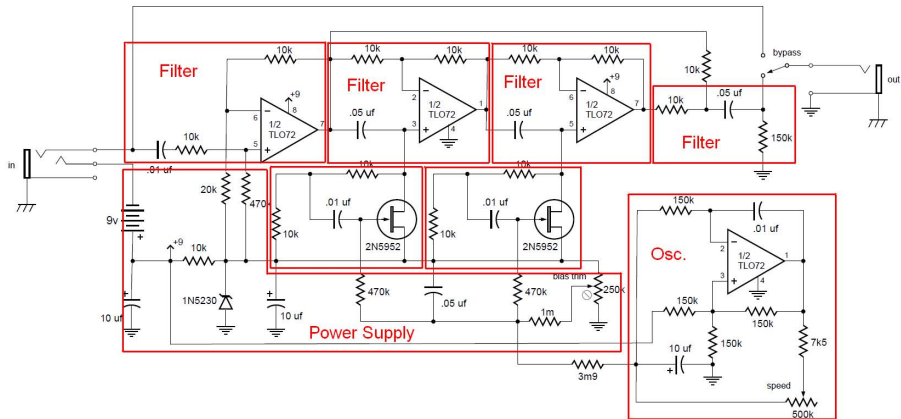Analog phaser effect – reduction of the model



Analog phaser effect – Real-time implementation

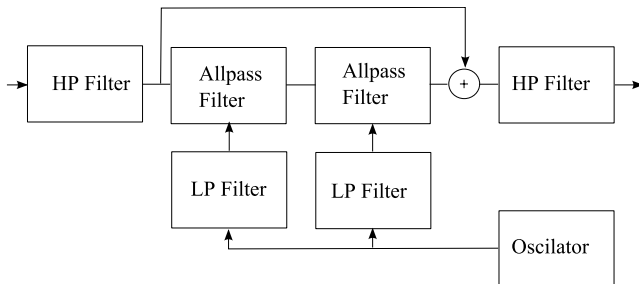- Four linear time-variable digital filters of first order and one summation in signal path
- Two linear digital filters of first order in parameter path
- Oscillator




Nonlinear models of analog effects

- Some analog audio effects are highly nonlinear
 - Guitar Distortion and Overdrive effect pedals
 - Guitar amplifiers
 - the goal of the effect is to produce higher harmonics and distort the signal
- Some effects have unwanted nonlinear distortion
 - Dynamic range controllers
 - Circuits with BJT and FET transistors


Techniques for modeling of nonlinear audio effect

- Static waveshaping
 - static nonlinear mapping from the input variable to the output variable
 - dynamic nonlinear systems are modeled by cascade of linear filters and nonlinear function
- Dynamic modeling
 - Nonlinear wave digital filters
 - Nonlinear state-space models
 - Nonlinear differential equations
- Require numerical solution of the model and are suitable for simple circuits
 - approximation of the solution
 - division into blocks


Example – Guitar tube preamp

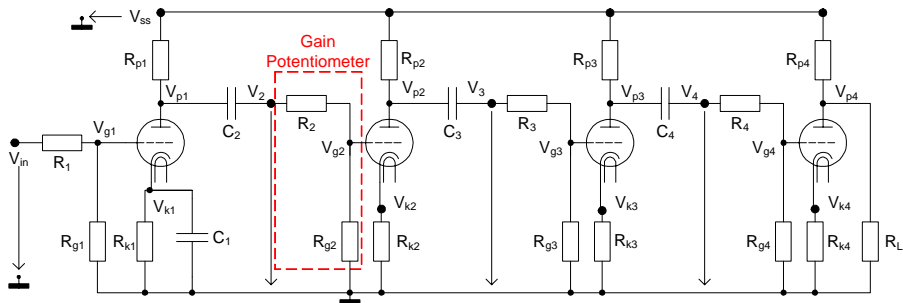

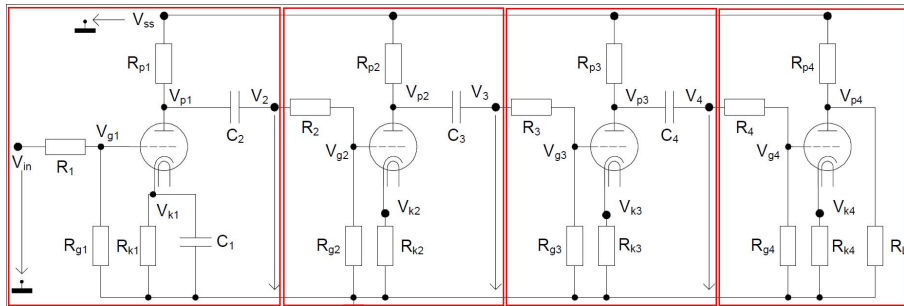Guitar tube preamp – division into blocks



Guitar tube preamp – one tube stage

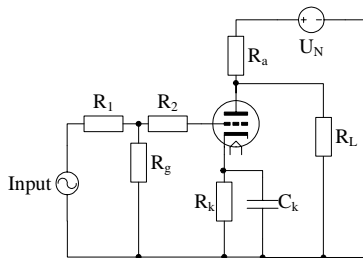

$$0 = G_2 \frac{U_{in} G_1 + U_g G_2}{G_1 + G_g + G_2} - U_g G_2 - i_g$$

$$0 = U_{c1m} - U_c + \frac{U_k G_k - i_a - i_g}{C_k f_s} \quad (1)$$

$$0 = U_N G_a - U_a G_a - U_a G_L - i_a$$


Precomputation for input variables: U_{in} , U_{c1m}

$$U_g = U_{Gapprox}(U_{in}, U_{c1m})$$

$$U_k = U_{Kapprox}(U_{in}, U_{c1m})$$

$$U_a = U_{Aapprox}(U_{in}, U_{c1m}) \quad (2)$$

One tube stage – approximation

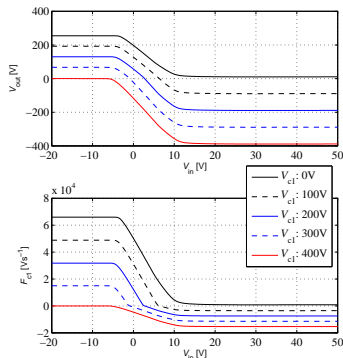



Update of the state variable:

$$\begin{aligned}
 U_{c1m} &= U_{c1m} + \frac{U_k G_k - i_a - i_g}{C_k f_s} \\
 &= U_{c1m} + T_S U_{C1approx}(U_{in}, U_{c1m})
 \end{aligned} \tag{3}$$

Final implementation:


$$\begin{aligned}
 U_a &= U_{Aapprox}(U_{in}, U_{c1m}) \\
 U_{c1m} &+ T_S U_{C1approx}(U_{in}, U_{c1m})
 \end{aligned} \tag{4}$$

Wrong impedance matching

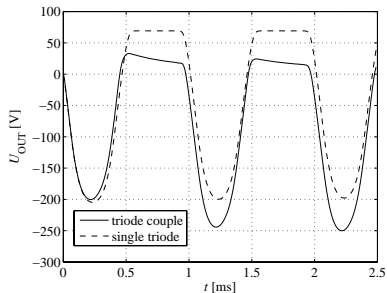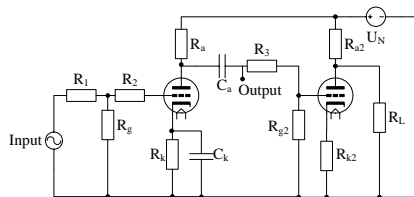


Modified blockwise method

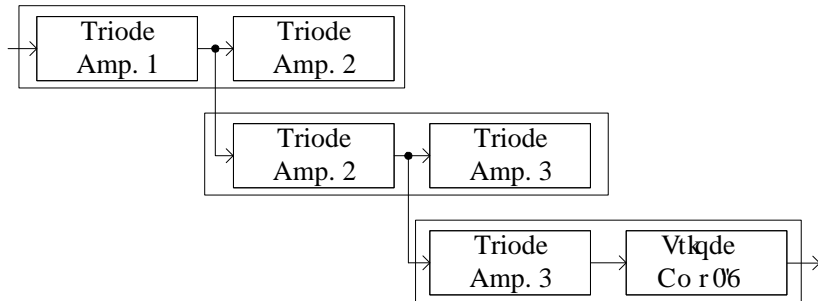
- designed to simulate nonlinear mutual interaction
- computational complexity is higher than with simple division into blocks, but still much lower than simulation of the whole system



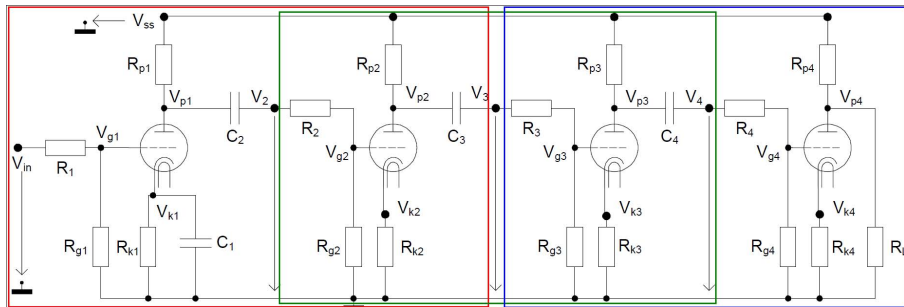Guitar tube preamp – new division into blocks



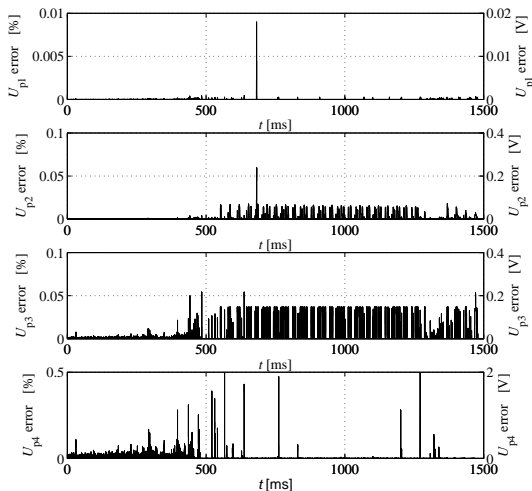Guitar tube preamp – error signal between numerical solution and approximation and blockwise method



Was the simulation succesfull?

Thank you for your attention